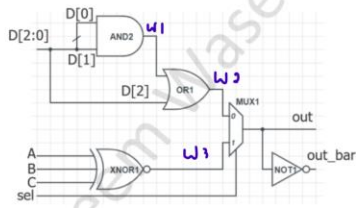


Abdelrahman Ahmed


TASK 1

 1)

- The design has 5 inputs and 2 outputs
- Randomize the stimulus in the testbench and make sure that the output is correct from the waveform



```
Welcome task_1.v x
V task_1.v > circuit_1
1 module circuit_1(D, A, B, C, Sel, out, out_bar);
2   input [2:0] D;
3   input A, B, C, Sel;
4   output out, out_bar;
5
6   and(w1, D[0], D[1]);
7   or(w2, D[2], w1);
8   xnor(w3, A, B, C);
9
10  assign out = (Sel == 0) ? w2 : w3;
11
12  assign out_bar = !out;
13
14  endmodule
```



-Test For 1-



TASK 2

2) Design a 4-bit priority encoder, the following truth table is provided where x is 4-bit input and y is a 2-bit output. Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

x3	x2	x1	x0	y1	y0
1	X	X	X	1	1
0	1	X	X	1	0
0	0	1	X	0	1
0	0	0	X	0	0

```
task_2.v > circuit_2
1  module circuit_2(input reg [3:0] x, output reg [1:0] y);
2
3  always @(x) begin
4      casez (x)
5          4'b000? : y = 2'b00;
6          4'b001? : y = 2'b01;
7          4'b01?? : y = 2'b10;
8          4'b1??? : y = 2'b11;
9          default : y = 2'b00;
10     endcase
11 end
12
13 endmodule
```



-Test For 2-

The image shows a Verilog testbench for a circuit, followed by its simulation results in a waveform viewer.

Verilog Code (task_2_tb.v):

```
1 module circuit_2_tb();
2   reg [3:0] x_tb;
3   wire [1:0] y_dut;
4   reg [1:0] y_expected;
5
6   circuit_2 test_circuit_2(x_tb, y_dut);
7
8   integer i;
9   initial begin
10    for (i=0; i<30; i=i+1) begin
11      x_tb = $random;
12      casez (x_tb)
13        4'b000? : y_expected = 2'b00;
14        4'b001? : y_expected = 2'b01;
15        4'b01?? : y_expected = 2'b10;
16        4'b1??? : y_expected = 2'b11;
17        default : y_expected = 2'b00;
18      endcase
19
20      #10
21      if (y_dut != y_expected)begin
22        $display("Error Unexpected output");
23        $stop;
24      end
25    end
26  end
27  initial begin
28    $monitor("x_tb = %b ---- y_dut = %b ---- y_expected = %b", x_tb, y_dut, y_expected);
29  end
30
31 endmodule
32
```

Simulation Results (Waveform Viewer):

The waveform viewer shows three signals: `/circuit_2_tb/x_tb` (4-bit), `/circuit_2_tb/y_dut` (2-bit), and `/circuit_2_tb/y_exp...` (2-bit). The signals are sampled at 4ns intervals. The first three samples show the expected output for the first three random inputs.

Time (ns)	x_tb (4-bit)	y_dut (2-bit)	y_expected (2-bit)
0	0000	00	00
10	0001	01	01
20	0010	10	10
30	0011	11	11
40	0100	00	00
50	0101	01	01
60	0110	10	10
70	0111	11	11
80	1000	00	00
90	1001	01	01
100	1010	10	10
110	1011	11	11
120	1100	00	00
130	1101	01	01
140	1110	10	10
150	1111	11	11
160	0000	00	00
170	0001	01	01
180	0010	10	10
190	0011	11	11
200	0100	00	00
210	0101	01	01
220	0110	10	10
230	0111	11	11
240	1000	00	00
250	1001	01	01
260	1010	10	10
270	1011	11	11
280	1100	00	00
290	1101	01	01
300	1110	10	10
310	1111	11	11

TASK 3

3) Design a decimal to BCD "Binary Coded Decimal" encoder has 10 input lines D0 to D9 and 4 output lines Y0 to Y3. Below is the truth table for a decimal to BCD encoder. Output should be held LOW if none of the following input patterns is observed. Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

Input										Output			
D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

```

V task_3.v
V task_3.v > DecimalToBCD
1  module DecimalToBCD (
2      input [9:0] D,
3      output reg [3:0] Y
4  );
5      always @(*) begin
6          case (D)
7              10'b0000000001: Y = 4'b0000;
8              10'b0000000010: Y = 4'b0001;
9              10'b0000000100: Y = 4'b0010;
10             10'b0000001000: Y = 4'b0011;
11             10'b0000010000: Y = 4'b0100;
12             10'b0000100000: Y = 4'b0101;
13             10'b0001000000: Y = 4'b0110;
14             10'b0010000000: Y = 4'b0111;
15             10'b0100000000: Y = 4'b1000;
16             10'b1000000000: Y = 4'b1001;
17             default: Y = 4'b0000;
18         endcase
19     end
20 endmodule
21

```



-Test For 3 -

```

V task_3_tb.v > DecimalToBCD_tb
1  module DecimalToBCD_tb();
2
3      reg [9:0] D_tb;
4
5      reg [3:0] Y_expected;
6      wire [3:0] Y_dut;
7
8      DecimalToBCD DecimalToBC_dut (D_tb, Y_dut);
9
10     integer i;
11
12     initial begin
13         for (i=0; i<200; i=i+1) begin
14             D_tb = $random;
15             case (D_tb)
16                 10'b0000000001: Y_expected = 4'b0000;
17                 10'b0000000010: Y_expected = 4'b0001;
18                 10'b0000000100: Y_expected = 4'b0010;
19                 10'b0000001000: Y_expected = 4'b0011;
20                 10'b0000010000: Y_expected = 4'b0100;
21                 10'b0000100000: Y_expected = 4'b0101;
22                 10'b0001000000: Y_expected = 4'b0110;
23                 10'b0010000000: Y_expected = 4'b0111;
24                 10'b0100000000: Y_expected = 4'b1000;
25                 10'b1000000000: Y_expected = 4'b1001;
26                 default: Y_expected = 4'b0000;
27             endcase
28             #10
29             if (Y_expected != Y_dut) begin
30                 $display("Error, Not matched");
31                 $stop;
32             end
33         end
34     end
35     initial begin
36         $monitor("D_tb = %b, Y_expected = %b, Y_dut = %b", D_tb, Y_expected, Y_dut);
37     end
38
39 endmodule
40

```

	Msgs	
<div> <div>+</div> <div> <div>D_tb</div> <div>Y_expected</div> <div>Y_dut</div> </div> </div>	<div>-No Data-</div> <div>-No Data-</div> <div>-No Data-</div>	

```

# D_tb = 0000101101, Y_expected = 0000, Y_dut = 0000
# D_tb = 0011000111, Y_expected = 0000, Y_dut = 0000
# D_tb = 0000101110, Y_expected = 0000, Y_dut = 0000
# D_tb = 0000001000, Y_expected = 0011, Y_dut = 0011
# D_tb = 0100011100, Y_expected = 0000, Y_dut = 0000
# D_tb = 1011111101, Y_expected = 0000, Y_dut = 0000
# D_tb = 1100101001, Y_expected = 0000, Y_dut = 0000
# D_tb = 0000011100, Y_expected = 0000, Y_dut = 0000

```

TASK 4

4) Implement N-bit adder using Dataflow modeling style

- The design takes 2 inputs (A, B) and the summation is assigned to output (C) ignoring the carry.
- Parameter N has default value = 1.
- Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

```
task_4.v > NBitAdder
1 module NBitAdder #(parameter W = 1)(
2     input [W-1:0] A, B,
3     output [W:0] C
4 );
5
6     assign C = A + B;
7
8 endmodule
```

I did one Extra bit for overflow.

	Msgs	
/NBitAdder/A	1'h1	
/NBitAdder/B	1'h1	
/NBitAdder/C	2'h2	
		1 2

-Test for 4 -

task_3.v
task_3_tb.v
task_4.v
test_4_tb.v
tb_bcd.v

```

1  module NBitAdder_tb();
2      parameter W = 1;
3      reg [W-1:0] A_tb, B_tb;
4      reg [W:0] C_expected;
5      wire [W:0] C_dut;
6
7      NBitAdder NBitAdder_test(A_tb, B_tb, C_dut);
8
9      integer i;
10     initial begin
11         for (i = 0; i < 10; i = i + 1) begin
12             A_tb = $random;
13             B_tb = $random;
14             C_expected = A_tb + B_tb;
15             #10
16             if (C_dut != C_expected) begin
17                 $display("Error outputs not matched");
18                 $stop;
19             end
20         end
21     end
22     initial begin
23         $monitor("A_tb = %b, B_tb = %b, C_expected = %b, C_dut = %b", A_tb, B_tb, C_expected, C_dut);
24     end
25
26 endmodule

```

	A_tb	B_tb	C_expected	C_dut
	1h1	1h0		
	2h1	2h1		
	2h1	2h1		

```

V$IM 46> run -all
# A_tb = 0, B_tb = 1, C_expected = 01, C_dut = 01
# A_tb = 1, B_tb = 1, C_expected = 10, C_dut = 10
# A_tb = 1, B_tb = 0, C_expected = 01, C_dut = 01
# A_tb = 1, B_tb = 1, C_expected = 10, C_dut = 10
# A_tb = 0, B_tb = 1, C_expected = 01, C_dut = 01
# A_tb = 1, B_tb = 0, C_expected = 01, C_dut = 01
# A_tb = 1, B_tb = 1, C_expected = 10, C_dut = 10
V$IM 47>


```


TASK 5

5) Design N-bit ALU that perform the following operations

- The design has 3 inputs and 1 output
- Instantiate the half adder from the previous question to implement the addition operation of the ALU
- For the subtraction, subtract B from A "A - B"
- Parameter N has default value = 4.
- Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.


Inputs		Outputs
opcode		Operation
0	0	Addition
1	0	Subtraction
0	1	OR
1	1	XOR

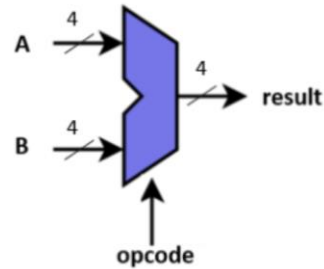

```


V task_5.v X V task_4.v
V task_5.v > ...
1 module Alu(A, B, op, out);
2     parameter W1 = 4;
3     input [W1-1:0] A, B;
4     input [1:0] op;
5     output reg [W1:0] out;
6
7     wire [W1:0] add_result;
8
9     NBitAdder #(W1) adder (
10         .A(A),
11         .B(B),
12         .C(add_result)
13     );
14
15     always @(*) begin
16         case (op)
17             2'b00: out = add_result;
18             2'b01: out = A | B;
19             2'b10: out = A - B;
20             2'b11: out = A ^ B;
21             default: out = 0;
22         endcase
23     end
24 endmodule
25

```

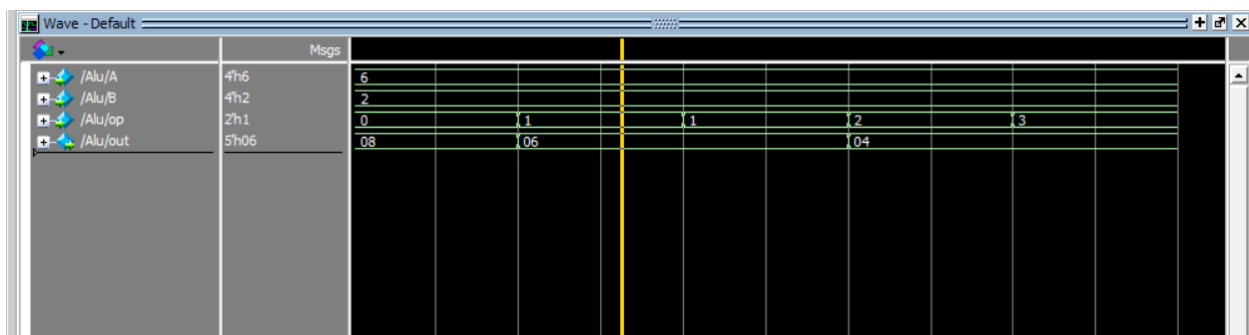

-Test for 5-

```
task_5.v task_5_tb.v x lab-1.v test.v task_4.v
V task_5_tb.v > Alu_tb
1 module Alu_tb();
2     parameter W1 = 4;
3     reg [W1-1:0] A_tb, B_tb;
4     reg [1:0] op_tb;
5     reg [W1:0] out_expected;
6     wire [W1:0] out_dut;
7
8     Alu_test(A_tb, B_tb, op_tb, out_dut);
9
10
11     integer i;
12     initial begin
13         for (i = 0; i < 100; i = i + 1) begin
14             A_tb = $random;
15             B_tb = $random;
16             op_tb = $random;
17
18             case (op_tb)
19                 2'b00: out_expected = A_tb + B_tb;
20                 2'b01: out_expected = A_tb | B_tb;
21                 2'b10: out_expected = A_tb - B_tb;
22                 2'b11: out_expected = A_tb ^ B_tb;
23                 default: out_expected = 0;
24             endcase
25
26             #10
27             if (out_expected != out_dut) begin
28                 $display("Error outputs not matched");
29                 $stop;
30             end
31         end
32     end
33     initial begin
34         $monitor("A_tb = %b, B_tb = %b, op_tb = %b, out_dut = %b, out_expected = %b", A_tb, B_tb, op_tb, out_dut, out_expected);
35     end
36 endmodule
```

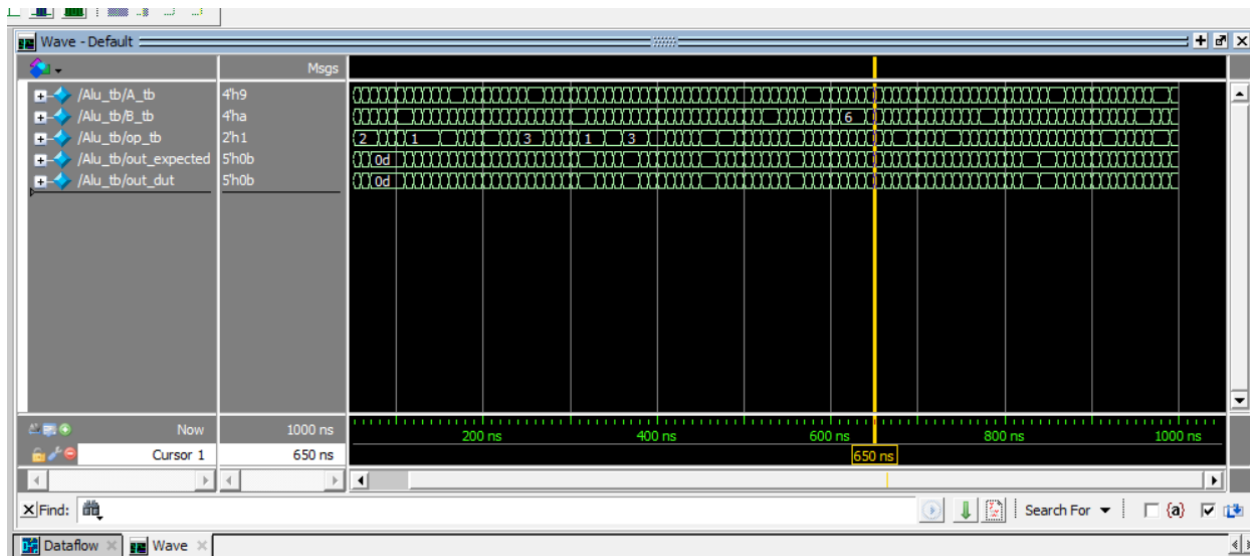


TASK 6

```

V task_6.v > Seven_Segment
1  module Seven_Segment #(parameter W = 4)
2      (input [W-1:0] A, B,
3      input [1:0] op,
4      input enable,
5      output reg [6:0] seg);
6      wire [W-1:0] alu_output;
7
8      Alu #(W) operations(A, B, op, alu_output);
9
10     always @(*) begin
11         if (!enable) begin
12             seg = 7'b0000000;
13         end
14         else begin
15             case (alu_output)
16                 4'h0: seg = 7'b1111110;
17                 4'h1: seg = 7'b0110000;
18                 4'h2: seg = 7'b1101101;
19                 4'h3: seg = 7'b1111001;
20                 4'h4: seg = 7'b0110011;
21                 4'h5: seg = 7'b1011011;
22                 4'h6: seg = 7'b1011111;
23                 4'h7: seg = 7'b1110000;
24                 4'h8: seg = 7'b1111111;
25                 4'h9: seg = 7'b1111011;
26                 4'hA: seg = 7'b1110111;
27                 4'hB: seg = 7'b0011111;
28                 4'hC: seg = 7'b1001110;
29                 4'hD: seg = 7'b0111101;
30                 4'hE: seg = 7'b1001111;
31                 4'hF: seg = 7'b1000111;
32                 default: seg = 7'b0000000;
33             endcase
34         end
35     end
36 end
37
38 endmodule

```

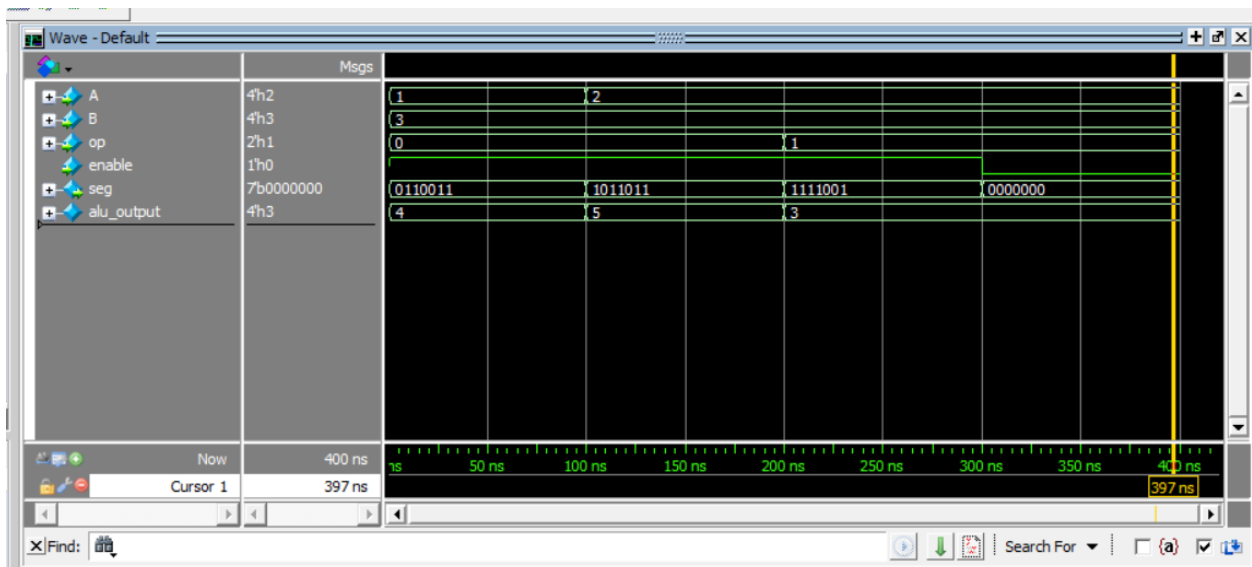

-Test for 6-

```

task_6_tb.v > Seven_Segment_tb
1  module Seven_Segment_tb();
2      parameter W = 4;
3      reg [W-1:0] A_tb, B_tb;
4      reg [1:0] op_tb;
5      reg enable_tb;
6      reg [6:0] seg_expected;
7      wire [6:0] seg_dut;
8      wire [W-1:0] alu_output;
9      Seven_Segment #(4) Seven_Segment_test(
10         A_tb, B_tb, op_tb, enable_tb, seg_dut);
11
12     Alu #(W) operations(A_tb, B_tb, op_tb, alu_output);
13
14     integer i;
15     initial begin
16         for (i = 0; i < 100; i = i + 1) begin
17             A_tb = $random;
18             B_tb = $random;
19             op_tb = $random;
20             enable_tb = 1;
21             #1;
22             case (alu_output)
23                 4'h0: seg_expected = 7'b1111110;
24                 4'h1: seg_expected = 7'b0110000;
25                 4'h2: seg_expected = 7'b1101101;
26                 4'h3: seg_expected = 7'b1111001;
27                 4'h4: seg_expected = 7'b0110011;
28                 4'h5: seg_expected = 7'b1011011;
29                 4'h6: seg_expected = 7'b1011111;
30                 4'h7: seg_expected = 7'b1110000;
31                 4'h8: seg_expected = 7'b1111111;
32                 4'h9: seg_expected = 7'b1111011;
33                 4'hA: seg_expected = 7'b1110111;
34                 4'hB: seg_expected = 7'b0011111;
35                 4'hC: seg_expected = 7'b1001110;
36                 4'hD: seg_expected = 7'b0111101;
37                 4'hE: seg_expected = 7'b1001111;
38                 4'hF: seg_expected = 7'b1000111;
39                 default: seg_expected = 7'b0000000;
40             endcase
41             #10
42             if (seg_dut != seg_expected) begin
43                 $display("Error outputs are not matched");
44                 $stop;
45             end
46         end
47     end
48
49     initial begin
50         $monitor("alu_output = %b, seg_expected = %b, seg_dut = %b", alu_output, seg_expected, seg_dut);
51     end
52
53 endmodule

```

