

By: Abdelrahmen Ahmed


{Extra}

1) A four-bit binary number is represented as A3A2A1A0, where A3, A2, A1, and A0 represent the individual bits and A0 is equal to the LSB. Design a logic circuit using Verilog that will produce a HIGH output whenever the binary number is greater than 0010 and less than 1000.


- The design takes 1 input A (4-bits) and output out (1-bit)

Verilog:

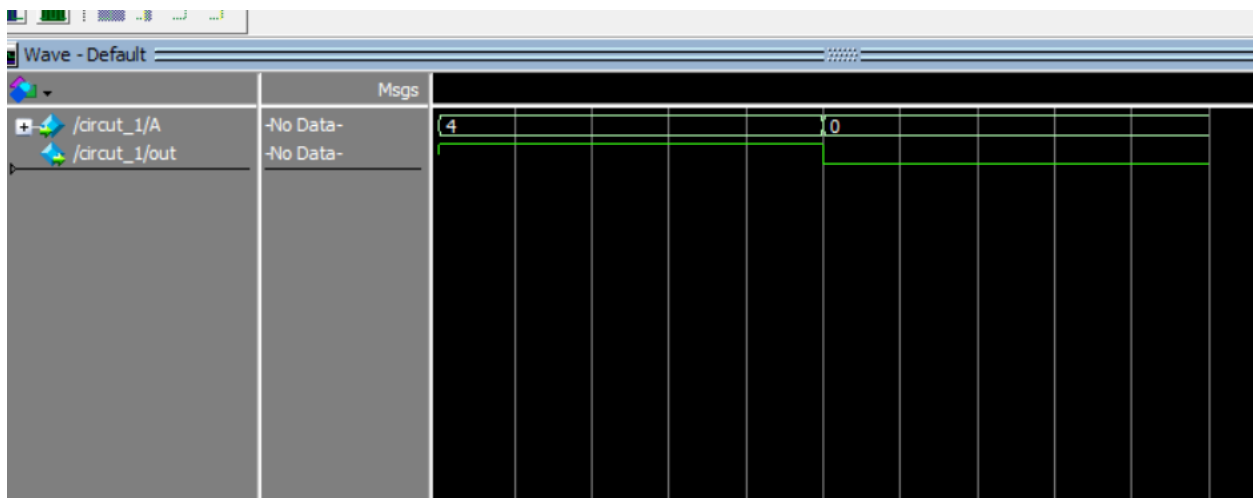
```
lab_1.v  X
Assignment_2 > lab_1.v > circuit_1
1  module circuit_1 (input [3:0] A, output out);
2
3  assign out = (A > 4'b0010) & (A < 4'b1000);
4
5  endmodule
```



2)

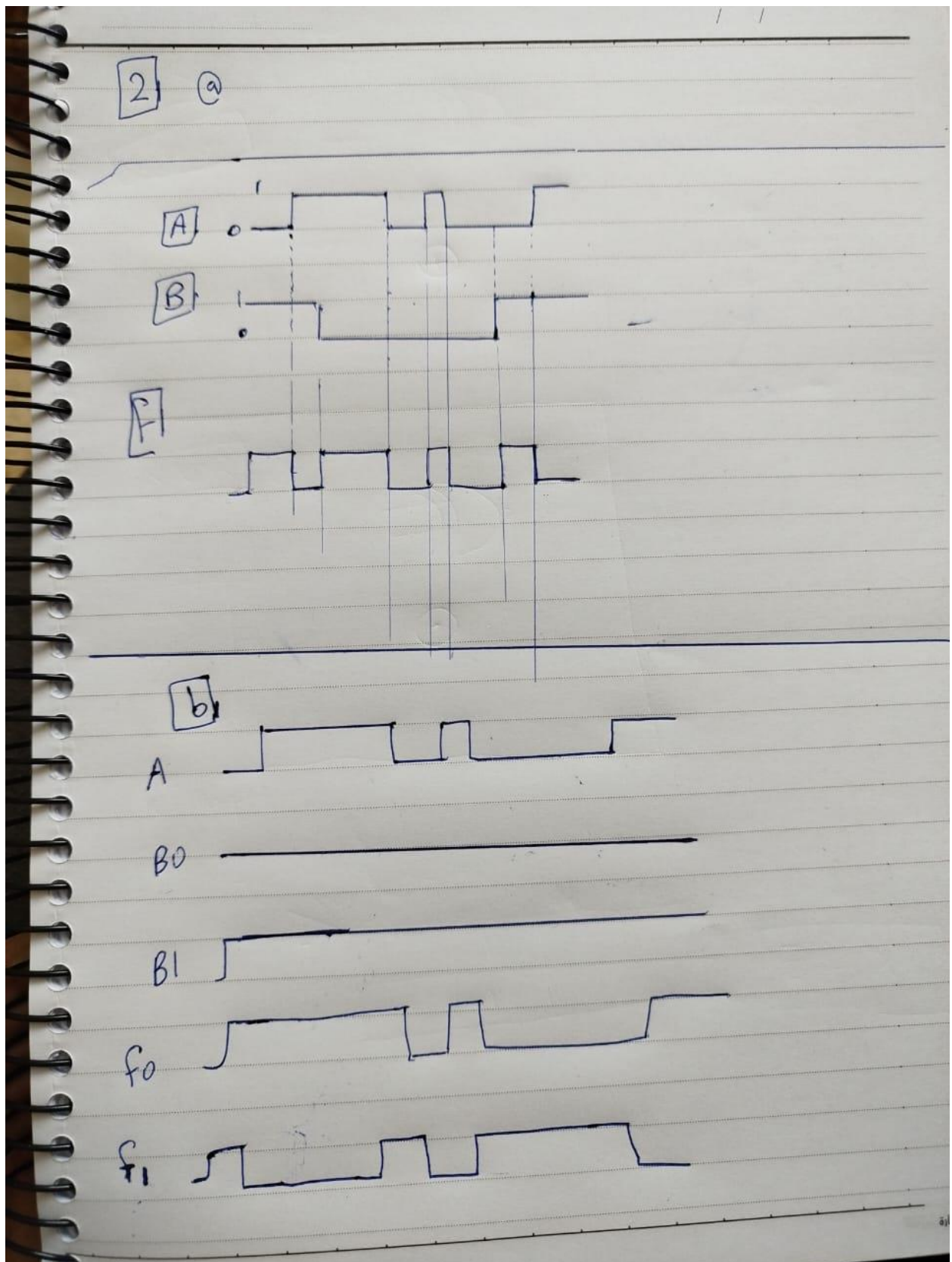

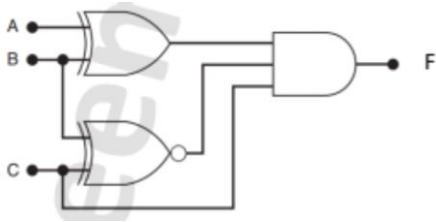3) Design the following circuit using Verilog and determine the input conditions needed to produce $F = 1$



Assignment_2 > V lab_Ex_3.v > circuit_3

```
1 module circuit_3(input A, B, C, output F);
2
3 wire W1, W2;
4
5 assign W1 = A ^ B;
6 assign W2 = B ~^ C;
7 assign F = W1 & W2 & C;
8
9 endmodule
```

	Msgs													
/circuit_3/A	-No Data-													
/circuit_3/B	-No Data-													
/circuit_3/C	-No Data-													
/circuit_3/F	-No Data-													

F will be 1 if

A = 0

B = 1

C = 1