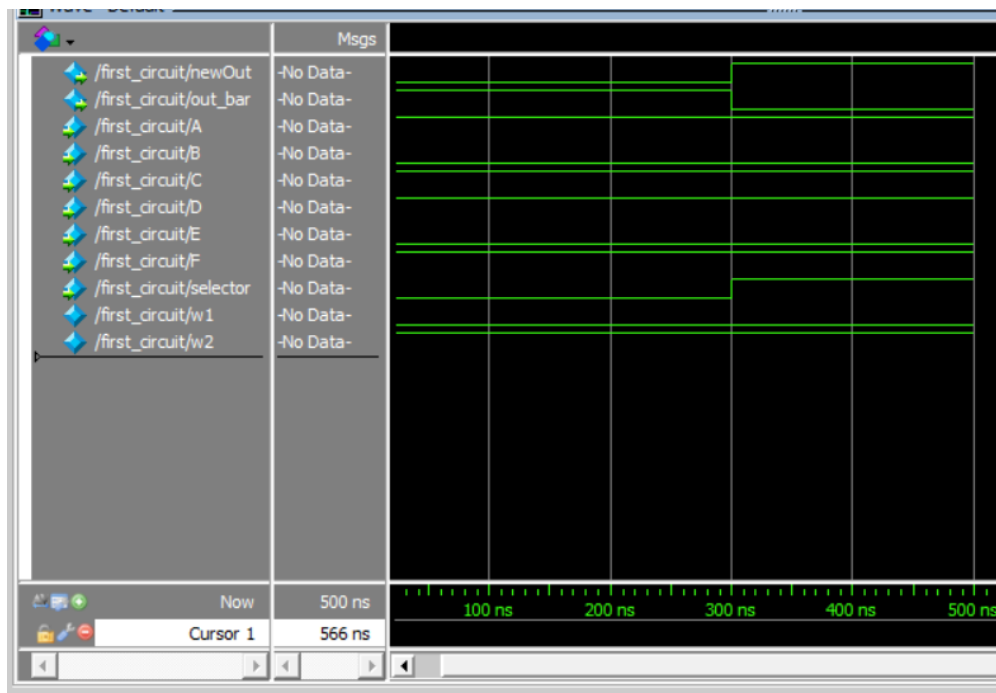


By: Abdelrahman Ahmed Sayed

First circuit

```
V first_question.v x V mux2.v
Assignment_1 > V first_question.v > first_circuit
1 module first_circuit (output newOut, out_bar, input A, B,C,D,E,F, selector);
2
3 wire w1, w2 ;
4
5 assign w1 = A && B && C;
6 assign w2 = D ~^ E ~^ F;
7
8 mux2 m(.out(newOut), .in0(w1), .in1(w2), .sel(selector));
9
10 assign out_bar = !newOut;
11
12 endmodule
```

```
V first_question.v x V mux2.v
Assignment_1 > V mux2.v > mux2
1 module mux2(in0, in1, sel, out);
2 input in0, in1, sel;
3 output out;
4 assign out = (sel == 1)? in1: in0;
5
6 endmodule
```




second circuit

```
mux2.v first_question.v second_question.v X
second_question.v > four_bit_adder
1 module four_bit_adder (input [3:0] A, B, output [3:0] C);
2
3 assign C = A + B;
4
5 endmodule
```

Wave - Default		Msgs	
+	/four_bit_adder/A	4'h0	2
	/four_bit_adder/B	4'h0	3
	/four_bit_adder/C	4'h0	5

Third circuit



```
mux2.v lab_1.v lab_3.v lab_2.v
Assignment_1 > lab_3.v > ...
1  module decoder(input A0, A1, output D0, D1, D2, D3);
2
3  assign D0 = (A1 == 0 && A0 == 0) ? 1 : 0;
4  assign D1 = (A1 == 0 && A0 == 1) ? 1 : 0;
5  assign D2 = (A1 == 1 && A0 == 0) ? 1 : 0;
6  assign D3 = (A1 == 1 && A0 == 1) ? 1 : 0;
7
8  endmodule
9  |
```

 

fourth circuit

```
1 module Even_parity_bit(input [7:0] A, output [8:0] out);
2
3 wire parity_bit;
4 assign parity_bit = ^A;
5 assign out = {A, parity_bit};
6
7 endmodule
```

first wave

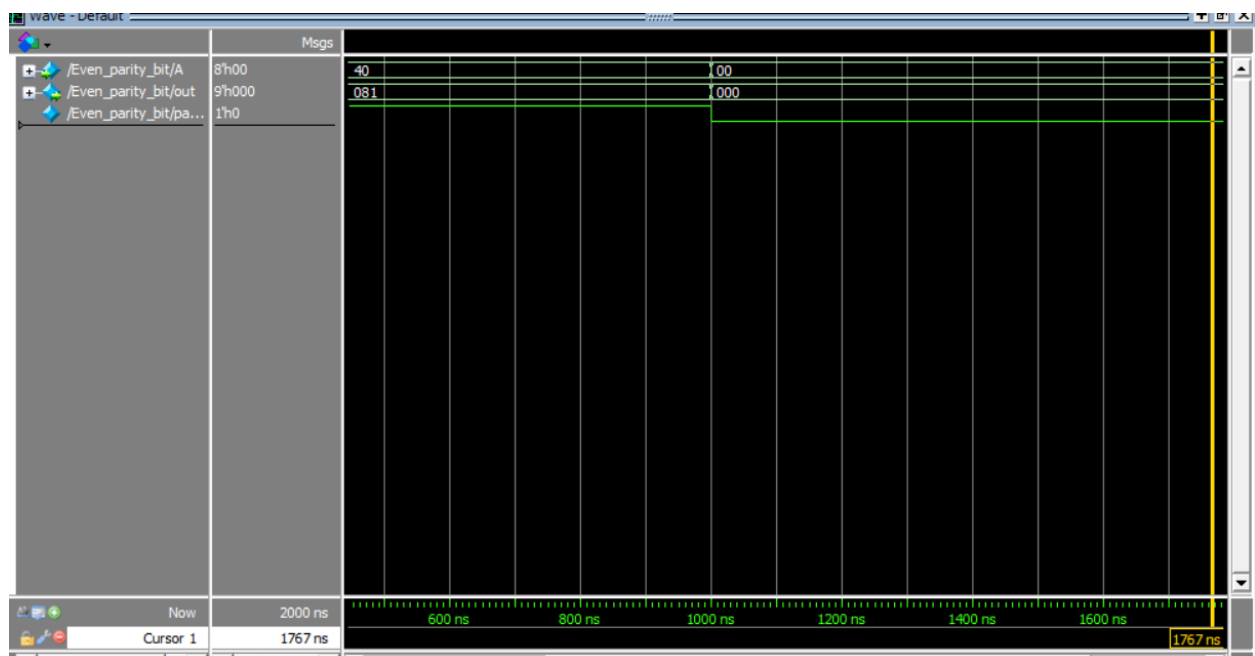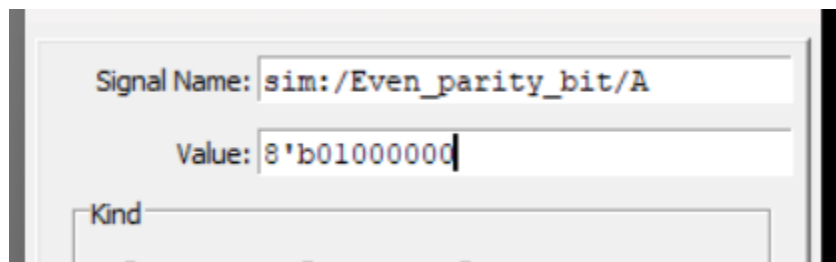

5 circuit

```
Assignment_1 > lab_5.v > ...  
1  module Comparator (  
2  input [3:0] A, B, output A_greaterthan_B, output A_equals_B, output A_lessthan_B);  
3  
4  assign A_greaterthan_B = (A > B) ? 1'b1 : 1'b0;  
5  assign A_equals_B = (A == B) ? 1'b1 : 1'b0;  
6  assign A_lessthan_B = (A < B) ? 1'b1 : 1'b0;  
7  
8  endmodule
```

